
Basic Electricity

BOPINDER (“BOP”) PHULL



Appalachian Underground Corrosion Short Course

Chapter 1 – Basic Electricity

- **Introduction**
- **Electrical Fundamentals**
 - **Physical Matter**
 - **Two General Types of Electricity**
- **Basic Terms**
- **Ohm's Law**
- **Basic Electrical Circuit**
- **Series Electrical Circuit**
- **Parallel Electrical Circuit**
- **Combination Circuits**



Introduction

- **This chapter covers:**
 - **Kinds of electricity encountered in corrosion and corrosion-control work**
 - **Explanation of various applicable electrical terms**
 - **How the electrical units represented by these terms interact**
 - **How the electrical units apply to various types of electrical circuits**



Introduction

- **Important to understand the principles in this chapter to fully comprehend the other chapters in the Basic Course**



Physical Matter

- **Substance that occupies space and has mass**
 - **Solids**
 - **Liquids**
 - **Gases**
- **Whatever the form, matter is made up of chemical elements**
- **Electrically conductive matter can allow passage of electricity**



Corrosion Fundamentals

- **Corrosion of a metal or alloy is a natural process in moist air, water, soil, etc.**
- **Metals are extracted from their ores in the earth's crust**
- **Corrosion returns metals to their natural state**
- **Corrosion of metals and alloys involves flow of electrical current**



For example, let's review how steel is made

- 1st step - Mining of Iron Ore (iron oxide)



How steel is made ... continued

- 2nd step - Smelting in blast furnace to convert iron-oxide to iron
- $\text{FeO} + \text{C} \longrightarrow \text{Fe} + \text{CO}$



Why steel corrodes

Natural process which returns metal to its native state

Iron ore, e.g. iron-oxide
(lower energy, stable state)



Note iron-oxide similarity \updownarrow




Corrosion in service environment
(iron-oxide corrosion products -
lower energy, stable state)

Smelting - to produce iron
(higher-energy, metastable state)




Steel mill products
(higher-energy, metastable state)

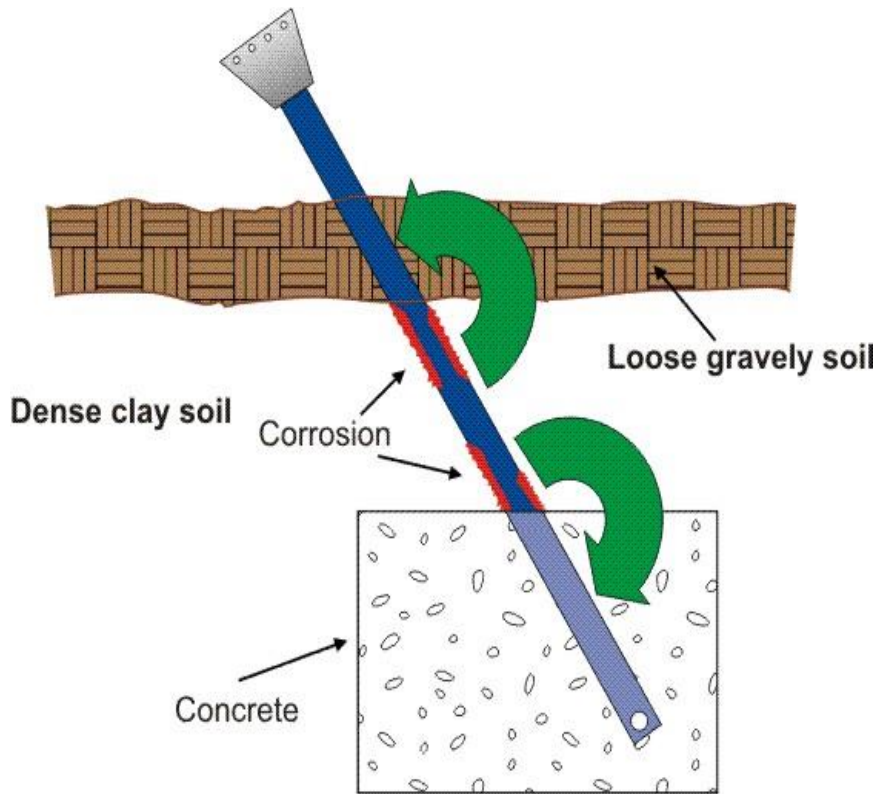Examples of Current Flow in Corrosion Cells




Dissimilar Environments

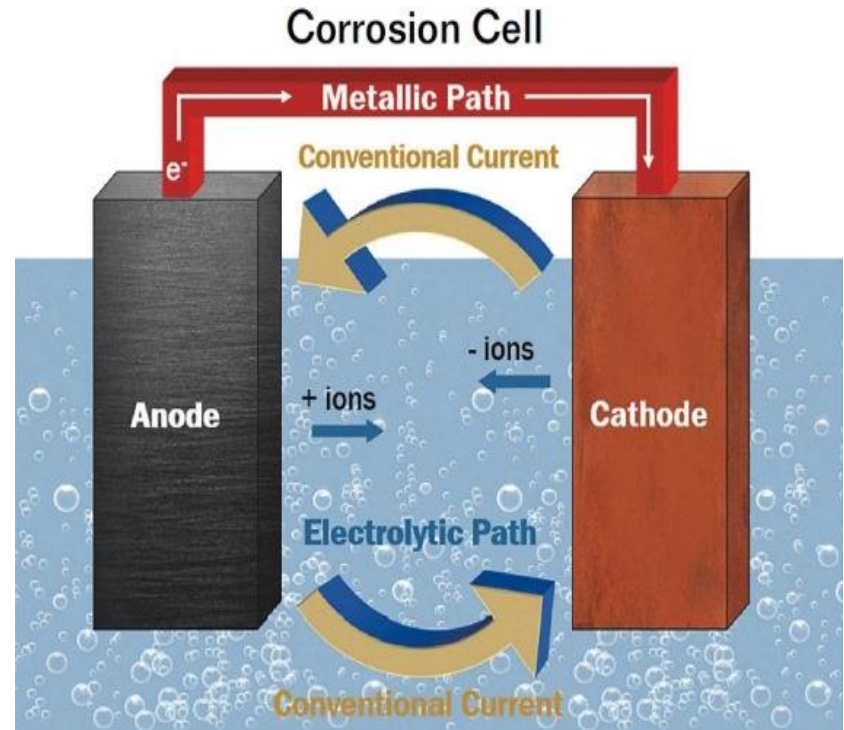


Dissimilar Metals

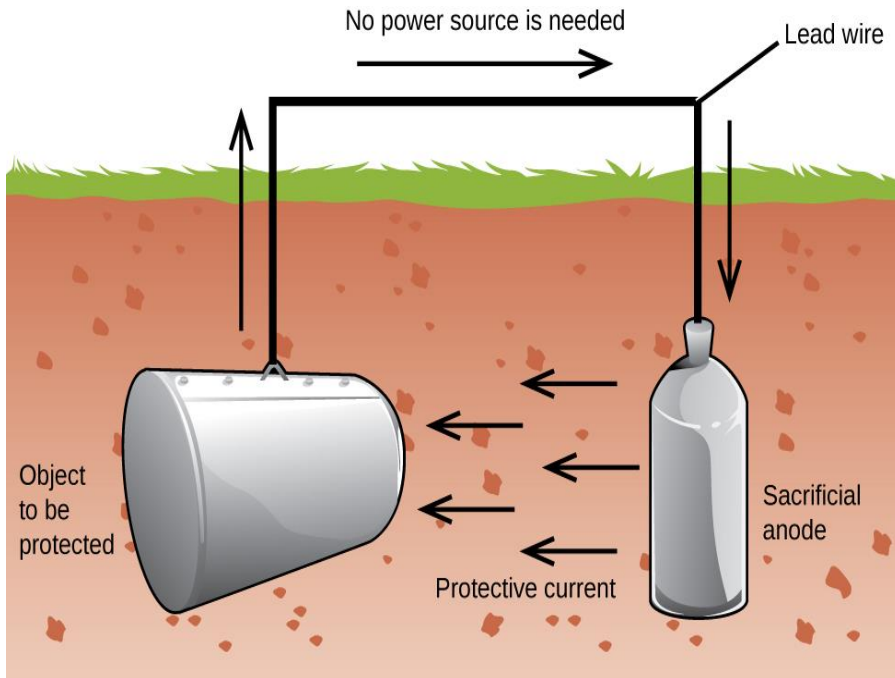Examples of Current Flow in Cathodic Protection




Galvanic Anode

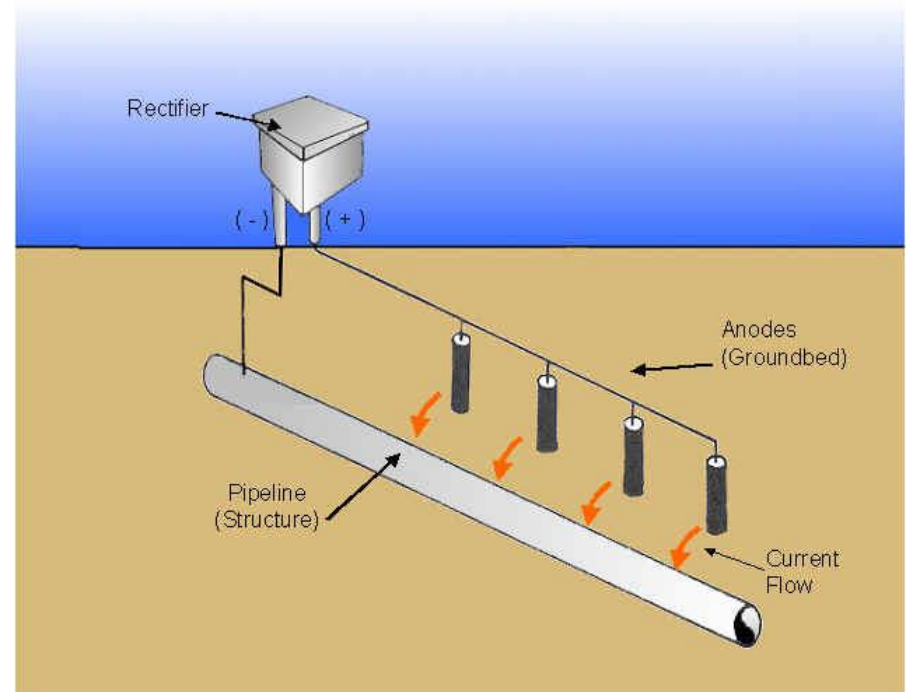

Impressed Current

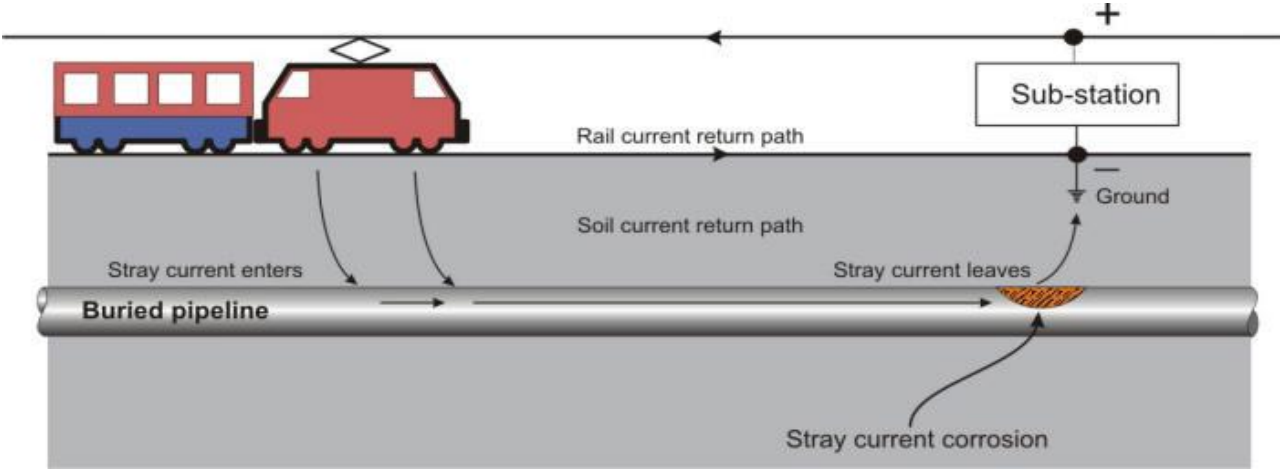Examples of Current Flow that can cause corrosion



Stray Currents

AC Interference



Physical Matter

- **What are Elements ?**
 - **Primary constituents of matter**
 - **Cannot be broken down into simpler substances**
 - **Examples of elements**
 - **Hydrogen (chemical symbol H)**
 - **Iron (chemical symbol Fe)**
 - **Copper (chemical symbol Cu)**
 - **Oxygen (chemical symbol O)**




Atoms

- **Atoms are building blocks of chemical elements**
- **Each element distinguished by its Atomic Number**
 - **Number of Protons (+) in the nucleus**



Atom

Protons -
positive charge

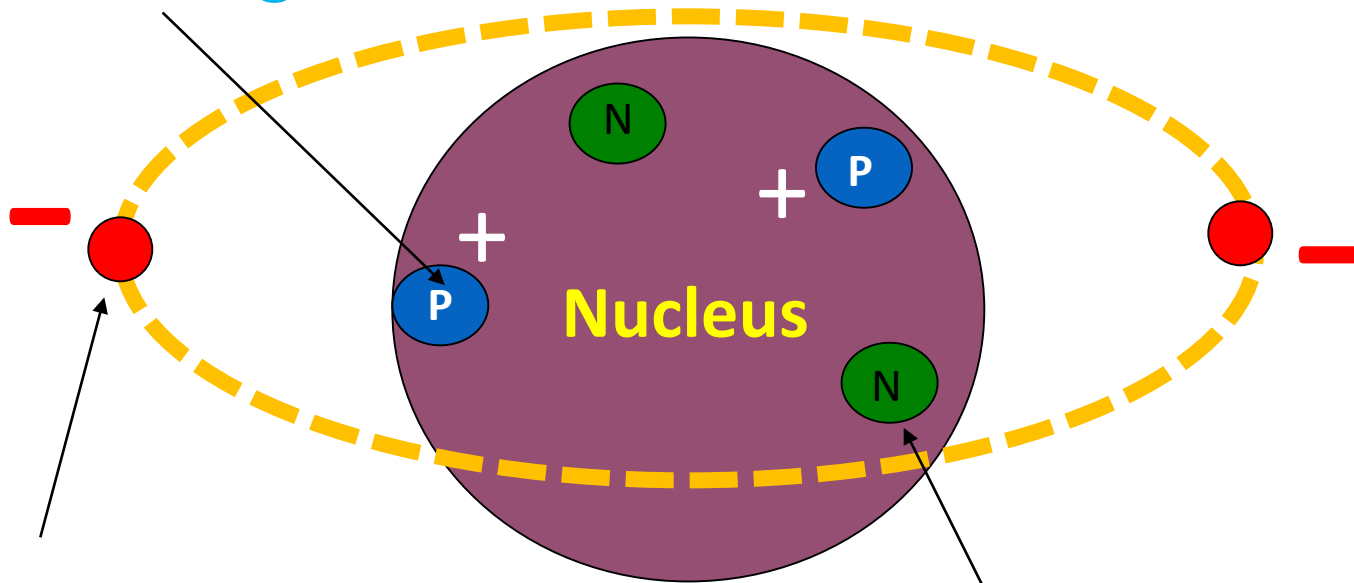

Electrons -
negative charge

Neutrons - no
charge

Periodic Table of the Elements

1 1A 1A 1 H Hydrogen 1.008	2 IIA 2A 4 Be Beryllium 9.012																	13 IIIA 3A 5 B Boron 10.811	14 IVA 4A 6 C Carbon 12.011	15 VA 5A 7 N Nitrogen 14.007	16 VIA 6A 8 O Oxygen 15.999	17 VIIA 7A 9 F Fluorine 18.998	18 VIIIA 8A 2 He Helium 4.003
3 1342 Li Lithium 6.941	1099 12 Mg Magnesium 24.305																	13 2519 Al Aluminum 26.982	14 3265 Si Silicon 28.086	15 white 280 5 15 P Phosphorus 30.974	16 444.61 16 S Sulfur 32.066	17 -101.5 17 Cl Chlorine 35.453	18 -185.847 18 Ar Argon 39.948
11 882.940 Na Sodium 22.990	19 759 K Potassium 39.098	3 IIIB 3B 21 Sc Scandium 44.956	4 IVB 4B 22 Ti Titanium 47.88	5 VB 5B 23 V Vanadium 50.942	6 VIB 6B 24 Cr Chromium 51.996	7 VIIB 7B 25 Mn Manganese 54.938	8 VIII 8 26 Fe Iron 55.933	9 VIII 8 27 Co Cobalt 58.933	10 VIII 8 28 Ni Nickel 58.693	11 IB 1B 29 Cu Copper 63.546	12 IIB 2B 30 Zn Zinc 65.39	31 2204 Ga Gallium 69.732	32 2833 Ge Germanium 72.61	33 616 SP 33 As Arsenic 74.922	34 685 34 Se Selenium 78.972	35 58.8 35 Br Bromine 79.904	36 -153.34 36 Kr Krypton 84.80						
37 688 Rb Rubidium 84.468	38 1382 Sr Strontium 87.62	39 3345 Y Yttrium 88.906	40 4409 40 Zr Zirconium 91.224	41 4744 41 Nb Niobium 92.906	42 4639 42 Mo Molybdenum 95.95	43 4265 43 Tc Technetium 98.907	44 4150 44 Ru Ruthenium 101.07	45 3695 45 Rh Rhodium 102.906	46 2963 46 Pd Palladium 106.42	47 2162 47 Ag Silver 107.868	48 767 48 Cd Cadmium 112.411	49 2072 49 In Indium 114.818	50 2602 50 Sn Tin 118.71	51 1587 51 Sb Antimony 121.760	52 988 52 Te Tellurium 127.6	53 184.4 53 I Iodine 126.904	54 -108.09 54 Xe Xenon 131.29						
55 671 Cs Cesium 132.905	56 1897 Ba Barium 137.327	57-71 Lanthanide Series	72 4603 72 Hf Hafnium 178.49	73 5458 73 Ta Tantalum 180.948	74 5555 74 W Tungsten 183.85	75 5596 75 Re Rhenium 186.207	76 5012 76 Os Osmium 190.23	77 4428 77 Ir Iridium 192.22	78 3825 78 Pt Platinum 195.08	79 2856 79 Au Gold 196.967	80 356.62 80 Hg Mercury 200.59	81 1473 81 Tl Thallium 204.383	82 1749 82 Pb Lead 207.2	83 1564 83 Bi Bismuth 208.980	84 962 84 Po Polonium [208.982]	85 337 85 At Astatine 209.987	86 -61.7 86 Rn Radon 222.018						
87 677 Fr Francium 223.020	88 1737 Ra Radium 226.025	89-103 Actinide Series	104 unknown 104 Rf Rutherfordium [261]	105 unknown 105 Db Dubnium [262]	106 unknown 106 Sg Seaborgium [266]	107 unknown 107 Bh Bohrium [264]	108 unknown 108 Hs Hassium [269]	109 unknown 109 Mt Meitnerium [268]	110 unknown 110 Ds Darmstadtium [269]	111 unknown 111 Rg Roentgenium [272]	112 unknown 112 Cn Copernicium [277]	113 unknown 113 Uut Ununtrium unknown	114 unknown 114 Fl Flerovium [289]	115 unknown 115 Uup Ununpentium unknown	116 unknown 116 Lv Livermorium [298]	117 unknown 117 Uus Ununseptium unknown	118 unknown 118 Uuo Ununoctium unknown						

Lanthanide Series

Actinide Series

57 3464 La Lanthanum 138.906	58 3443 Ce Cerium 140.115	59 3520 Pr Praseodymium 140.908	60 3074 Nd Neodymium 144.24	61 3000 Pm Promethium 144.913	62 1794 Sm Samarium 150.36	63 1529 Eu Europium 151.966	64 3273 Gd Gadolinium 157.25	65 3230 Tb Terbium 158.925	66 2567 Dy Dysprosium 162.50	67 2700 Ho Holmium 164.930	68 2868 Er Erbium 167.26	69 1950 Tm Thulium 168.934	70 1196 Yb Ytterbium 173.04	71 3402 Lu Lutetium 174.967
89 3198 Ac Actinium 227.028	90 4788 Th Thorium 232.038	91 4027 Pa Protactinium 231.036	92 4131 U Uranium 238.029	93 4174 Np Neptunium 237.048	94 3228 Pu Plutonium 244.064	95 2011 Am Americium 243.061	96 3100 Cm Curium 247.070	97 2627 Bk Berkelium 247.070	98 unknown 98 Cf Californium 251.080	99 unknown 99 Es Einsteinium [254]	100 unknown 100 Fm Fermium 257.095	101 unknown 101 Md Mendelevium 258.1	102 unknown 102 No Nobelium 259.101	103 unknown 103 Lr Lawrencium [262]

Alkali Metal	Alkaline Earth	Transition Metal	Basic Metal	Semimetal	Nonmetal	Halogen	Noble Gas	Lanthanide	Actinide
--------------	----------------	------------------	-------------	-----------	----------	---------	-----------	------------	----------

Physical Matter

- **What is a molecule ?**
 - **Molecule is chemical combination of two or more atoms**
 - **Examples:**
 - **Hydrogen gas (H₂)**
 - **Oxygen gas (O₂)**
 - **Nitrogen gas (N₂)**



Physical Matter

- **What is a compound ?**
 - **Molecule that contains at least two different elements**
 - **Examples:**
 - **Carbon dioxide (CO₂)**
 - **Hydrogen sulfide (H₂S)**
 - **Iron oxide (Fe₂O₃)**
 - **Copper sulfate (CuSO₄)**



Physical Matter

All compounds are molecules


but

Not all molecules are compounds

When an Atom becomes
an ION –

What Charge ????

Positive Charge!!!!

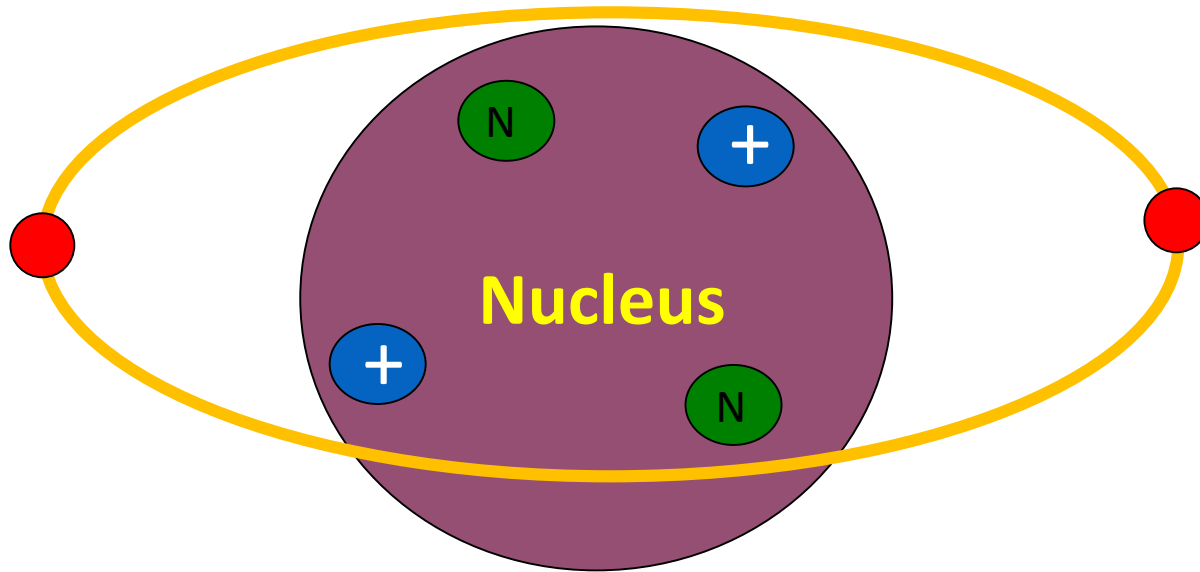

Ions

- **Two types of ions**
 - **Cations - Positively charged (+)**
 - **Anions – Negatively charged (-)**



Ions

- Ions form when atoms or molecules lose or gain excess electrons
 - $\text{Fe}^0 - 2\text{e}^- \longrightarrow \text{Fe}^{2+}$
 - Water : $\text{H}_2\text{O} \longrightarrow [\text{H}^+] + [\text{OH}^-]$
 - Sodium Chloride : $\text{NaCl} \longrightarrow [\text{Na}^+] + [\text{Cl}^-]$

Ions

- **Cations – Positively charged**
 - **Hydrogen ions – H^+**
 - **Sodium ions – Na^+**
 - **Calcium ions – Ca^{2+}**
 - **Ferrous ions – Fe^{2+}**
 - **Ferric ions – Fe^{3+}**
 - **Aluminum ions – Al^{3+}**





Ions

- **Anions – Negatively charged**
 - **Hydroxyl ions – OH⁻**
 - **Chloride ions – Cl⁻**
 - **Fluoride ions – F⁻**
 - **Sulfate ions – SO₄²⁻**
 - **Nitrate ions – NO₃⁻**
 - **Phosphate ions – PO₄²⁻**

Basic Corrosion Process

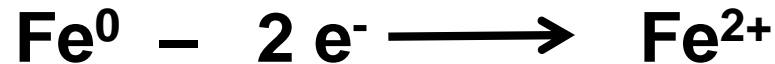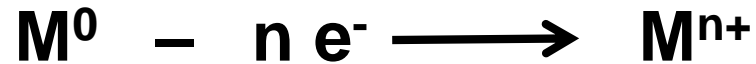- Oxidation - Metal ions go into solution at ANODIC areas by loss of electrons, e.g.



- Reduction - Occurs at CATHODIC areas by consumption of electrons, e.g.




Electrical Current


- **Electrical current involves the flow of electrons in the metallic path of an electrical circuit**
 - **Also known as electronic current**
- **Electrical current flow in electrolytes is due to movement of ions**
 - **Also known as ionic or electrolytic current**



Electrical Current

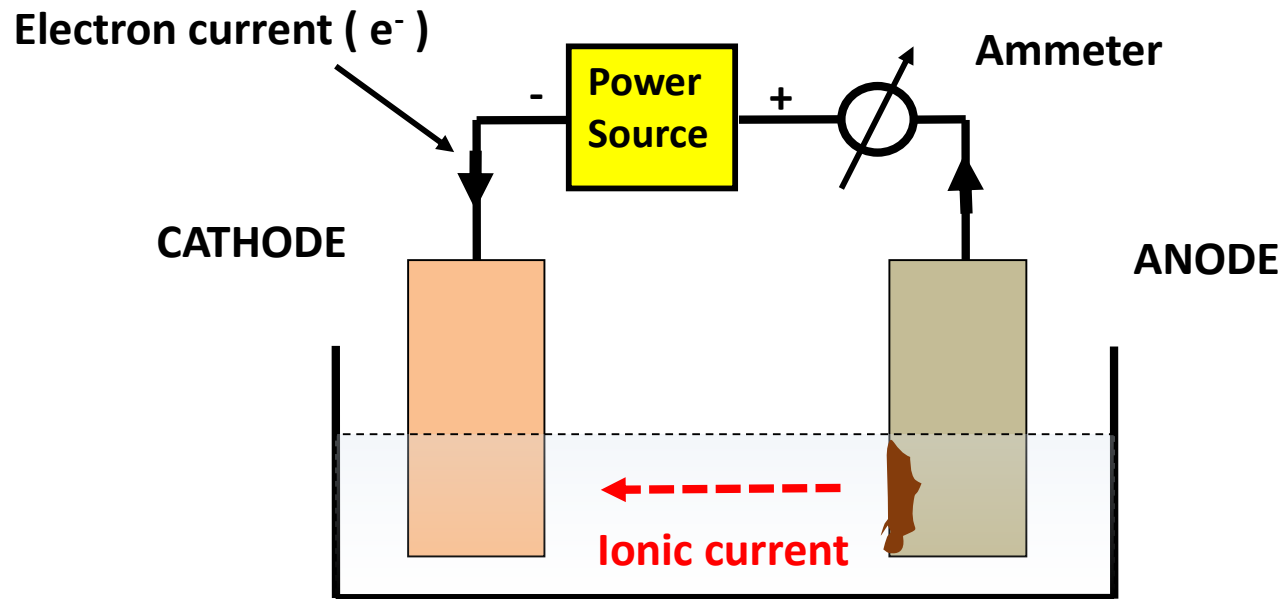

Conventional Current vs. Electron Flow

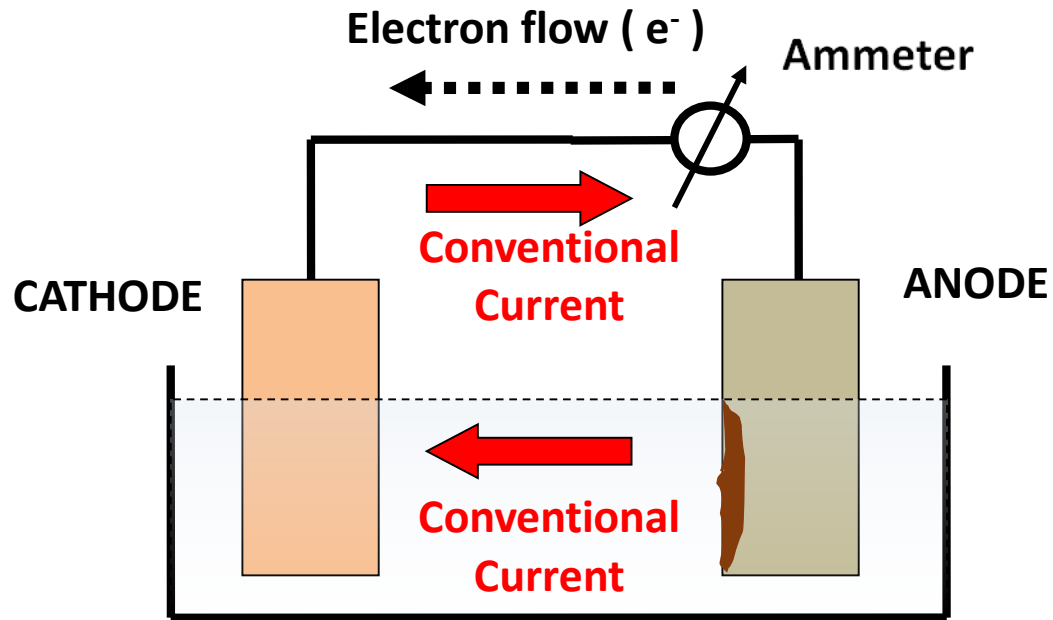

Electricity

- **Two types of electricity**
 - **Alternating Current (AC)**
 - **Direct Current (DC)**




Alternating Currents (AC)

- **Current flows first in one direction then in the opposite direction in accord with an established pattern**
- **Hertz – is a single cycle of the produced wave form**
- **Alternating current, in the US, has a frequency of 60 cycles per second, referred to as 60 Hertz (or 60 Hz)**



Alternating Current (AC)

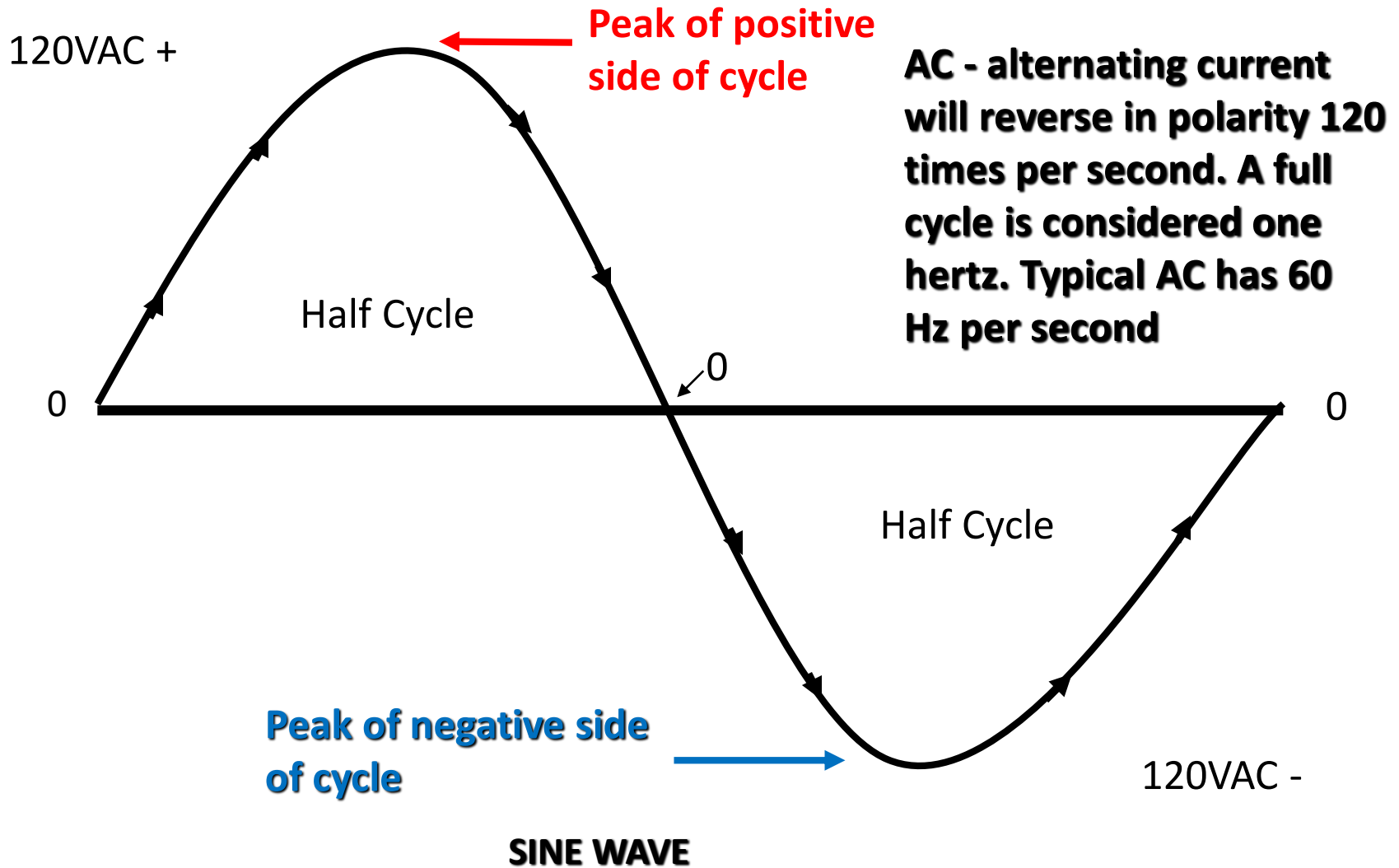

Significance of Alternating Current

- AC is a relatively insignificant factor as a cause of corrosion except in very special cases
- AC is used for a power source for Cathodic Protection such as rectifiers (which converts AC power to DC power) *Discussed more in Chapter 3 - Corrosion Control Methods*




Direct Current (DC)

- Flows in one direction
 - Examples
 - Flash light battery
 - Car battery



Direct Current (DC)

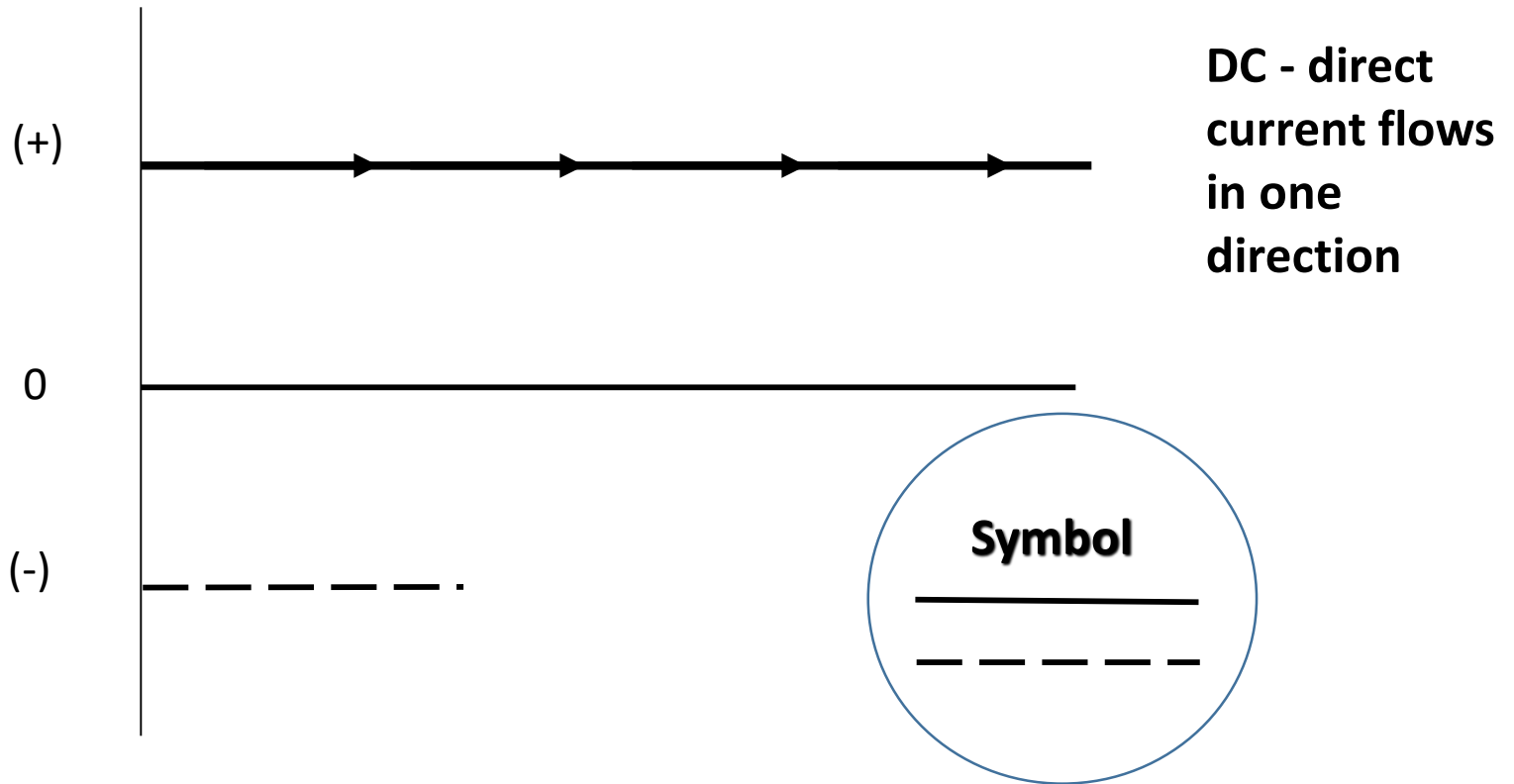


Significance of Direct Current

- **DC current is very important in the corrosion process**
 - **Involved in various types of corrosion cells (discussed in Chapter 2)**
 - **Involved in corrosion control – especially in cathodic protection (discussed in Chapter 3)**



Transformer Rectifier

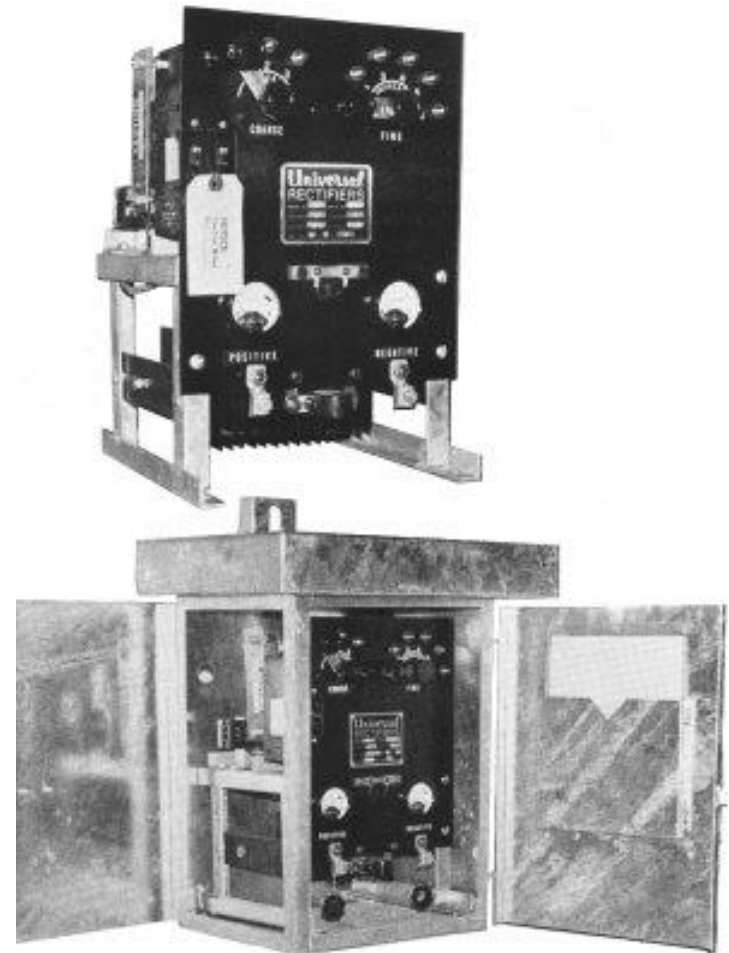Steps down AC voltage and
Converts AC to DC




Basic Terms

- **Typical terms and units involved in electrical circuits**
- **Voltage - Volts (V)**
- **Current - Amps (A)**
- **Resistance – Ohms (R)**



Potential Difference, Volts (V)

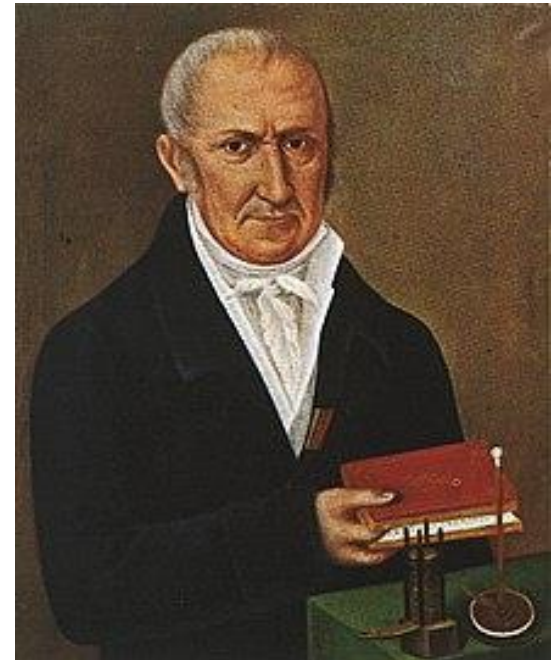- **Basic unit of electrical potential difference that causes an electrical current (electrons) to flow through a metallic circuit**
- **Named after Italian Physicist, Alessandro Volta**
- **Potential difference also known as Electromotive Force, (EMF), abbreviated as E**



Volts

One volt (V) is the basic unit, there are instances where much smaller units are easier to use

One millivolt (mV) is one thousands of a volt

One microvolt (μ V) is one millionth of a volt

– 1.000 volt = 1000 millivolts

– 0.100 volt = 100 millivolts

– 0.010 volt = 10 millivolts

– 0.001 volt = 1 millivolt

– 0.000001 volt = 1 microvolt

Volts

- In corrosion prevention work, sources of DC voltage used to provide cathodic protection current include:
 - Galvanic anodes
 - Zinc
 - Aluminum
 - Magnesium
 - Driving voltage of anodes may be measured in tenths of a volt or in millivolts.



Volts - continued

- **Other sources of DC voltage used to provide cathodic protection current include:**
 - **Higher capacity sources such as AC to DC rectifiers or DC generators of various types**
 - **Normally available in a wide range of voltages to match specific requirements**
 - **more fully discussed in chapter 3**



Current, Amperes (I)

- **Ampere is the basic unit of electrical current flow**

Named after French mathematician and physicist, Andre-Marie Ampere

- **Recall – Potential difference causes current flow in an electrical circuit**



Ampere – often abbreviated as amp

One amp (A) is the basic current flow unit, there are instances where very small fractions of an ampere may be involved in corrosion work

One milliamp (mA) is one thousandth of an ampere

One microamp (μA) is one millionth of a ampere

– 1.000 amp = 1000 milliamps

– 0.100 amp = 100 milliamps


– 0.010 amp = 10 milliamps

– 0.001 amp = 1 milliamp

– 0.000001 amp = 1 microampere

Resistance (R)

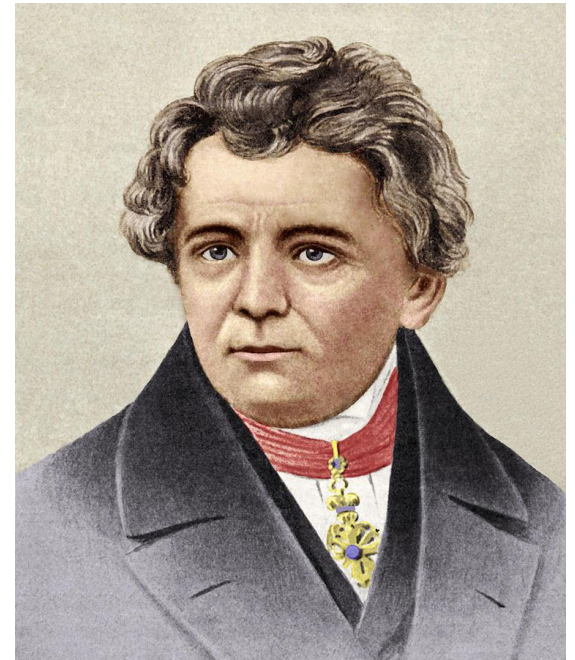- Ohm is the basic unit of resistance (R) to the flow of electrical current
- Named after German physicist and mathematician, Georg Simon Ohm
- Resistance (ohms) is the opposite of Conductance (mhos)



Resistance (R) - Ohms

- **Symbol Ω (omega) used commonly**

One ohm (R) is the basic unit of resistance. Other units may also be involved in corrosion work

R can have a wide range of values

- 10 megohms = 10,000,000 ohms
- 1 megohm = 1,000,000 ohms
- 10 kilohms = 10,000 ohms
- 1 kilohm = 1000 ohms
- **1 ohm = 1,000 milliohms**
- **0.1 ohm = 100 milliohms**
- **0.01 ohm = 10 milliohms**



Ohm's Law


- Current flow through a conductor between two points is proportional to the voltage across the two points

- Current (I) = $\frac{\text{Voltage (V)}}{\text{Resistance (R)}}$

Can be written in 3 ways:

- $I = \frac{V}{R}$ or $R = \frac{V}{I}$ or $V = I \times R$

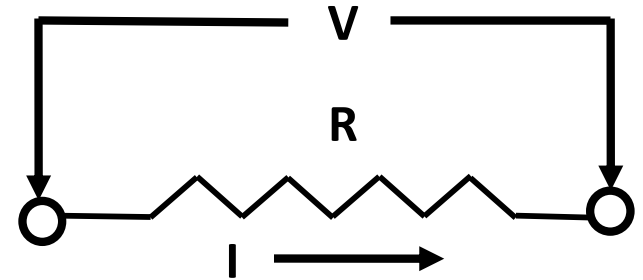- If any 2 of these are known the 3rd can be calculated




Ohm's Law - continued

- With a fixed driving voltage applied to an electrical circuit
 - The amount of current flowing through the circuit decreases as the circuit resistance increases
 - The amount of current flowing through the circuit increases as the circuit resistance decreases




Ohm's Law – Water Flow Analogy

Current (I)

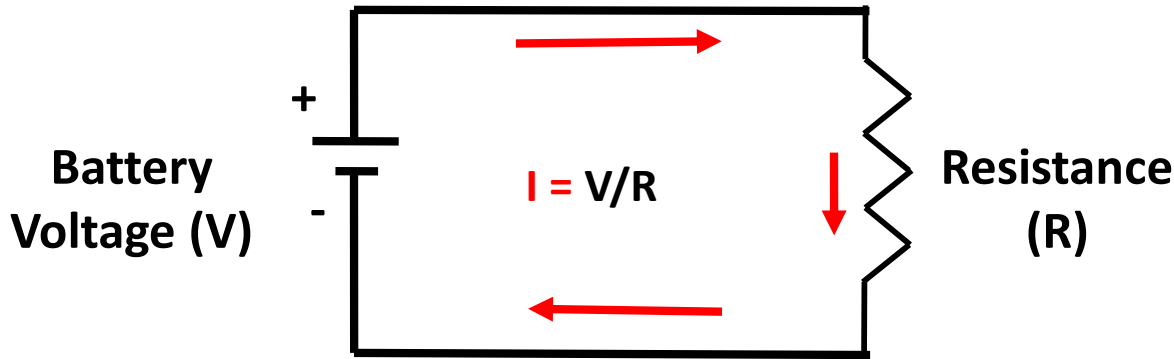

Water flow (gpm)

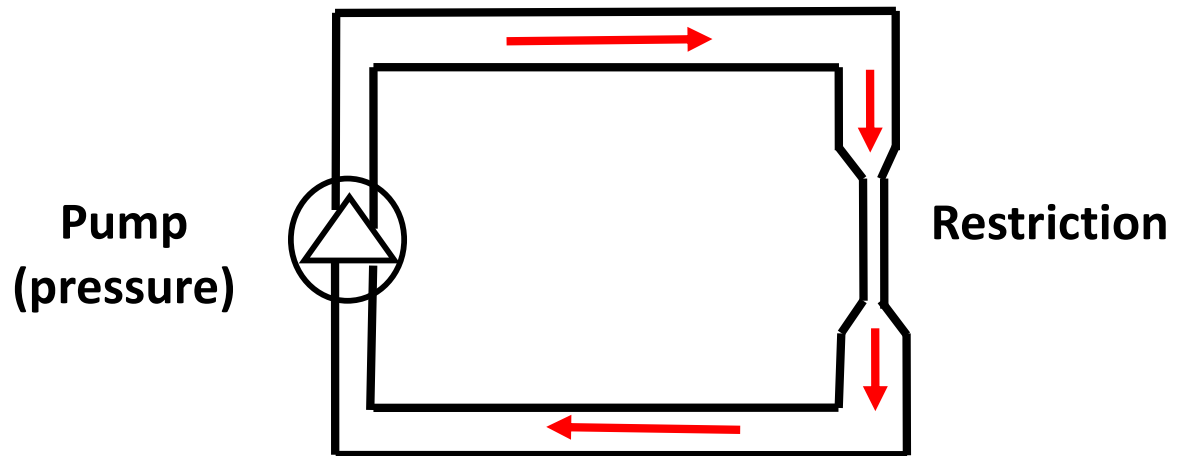

Resistance

- **Importance of resistance in corrosion and its control**
- **For example,**
 - **Insulators**
 - **Coatings**




Ohm's Law

E = Electromotive Force
Volts (V)

I = Current
Amps (A)

R = Resistance (Ω)

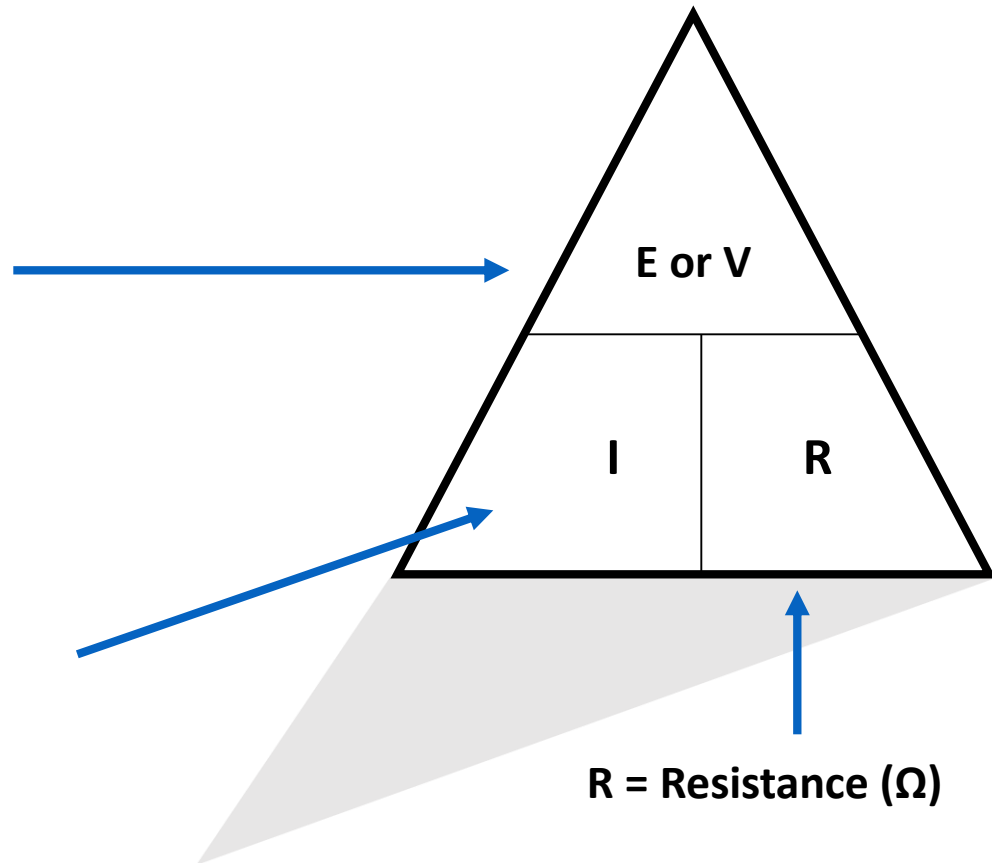


Resistivity

- **Resistivity is used to indicate the characteristic ability of a material to conduct electricity**
- **Can be applied to both metallic and non-metallic materials**
- **Commonly expressed as ohm-centimeters (ohm-cm); other units sometimes used are ohm-meters or ohm-ft**
- **Symbol used for resistivity - ρ (Greek letter rho)**



Resistivity

- Resistivity is a material property

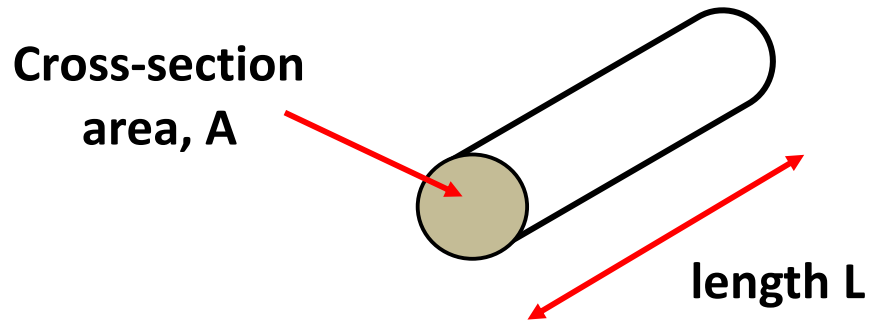

$$\text{Resistance, } R = \frac{\rho \times L}{A}$$

or

$$\text{Resistivity, } \rho = \frac{R \times A}{L}$$

Resistivity vs. Corrosivity

- Resistivity provides a general indication of corrosivity. Resistivity is opposite of conductivity
- Generally, lower resistivity (i.e. higher conductivity) of soil or water suggests more corrosion current can flow and hence higher corrosion rate
- Generally, higher resistivity (i.e. lower conductivity) of soil or water suggests less corrosion current can flow and hence lower corrosion rate



Resistivity vs. Corrosivity

Soil Resistivity (ohm-cm)	Corrosivity
< 2000	Severe
2000 - 5000	Moderately
5000 - 10,000	Low
> 10,000	Negligible

Resistivity

- **Most common reason for measuring resistivity of soils and waters is in design of Cathodic Protection (CP) systems**
 - **Design**
 - **Galvanic anode-to-electrolyte resistance**
 - **Ground bed design for impressed current system**




Resistivity Measurements

- Tools used for measuring resistivity of soils
 - Collins rod
 - Wenner Four-pin method – most commonly used in the field
 - Soil box
- For water – typically conductivity cell used
 - Conductivity can be converted to resistivity



Wenner 4-Pin Method


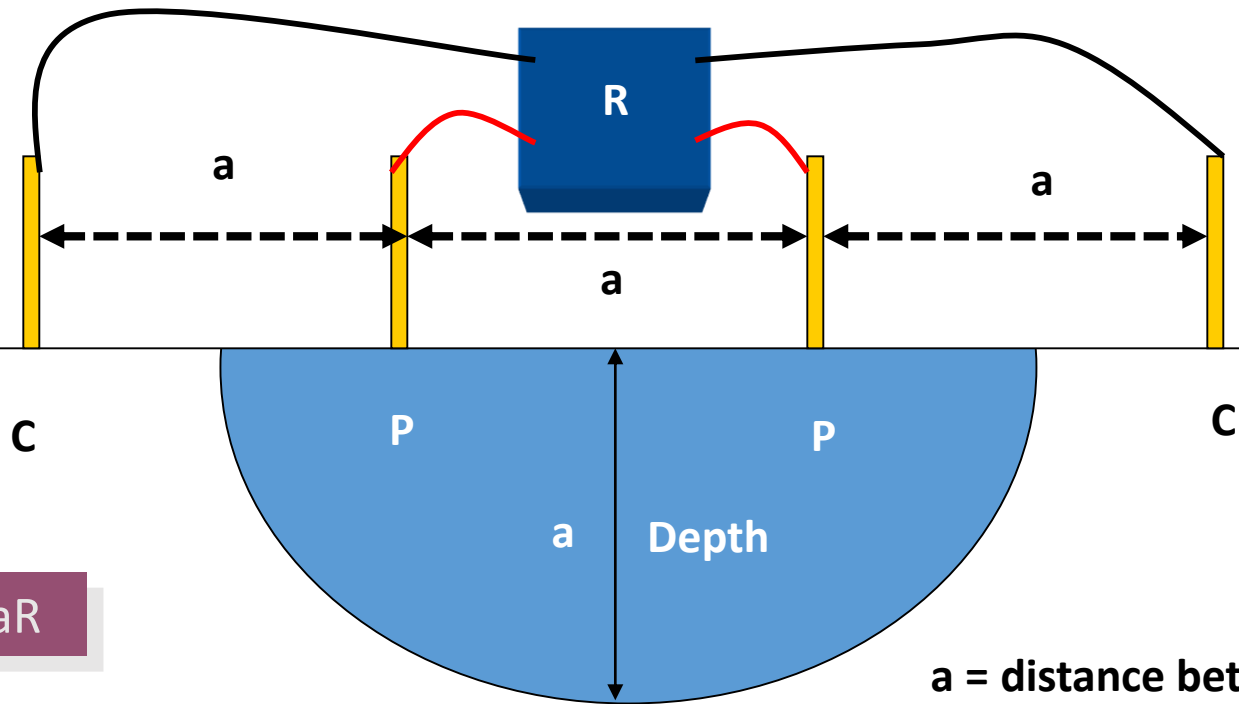


$$\rho = 191.5aR$$

Resistivity, ρ (ohm-cm)
Pin separation, a (ft)
Resistance, R (ohms)

Measured average resistivity to depth
corresponding to distance between pins

4-Pin Soil Resistivity Tester

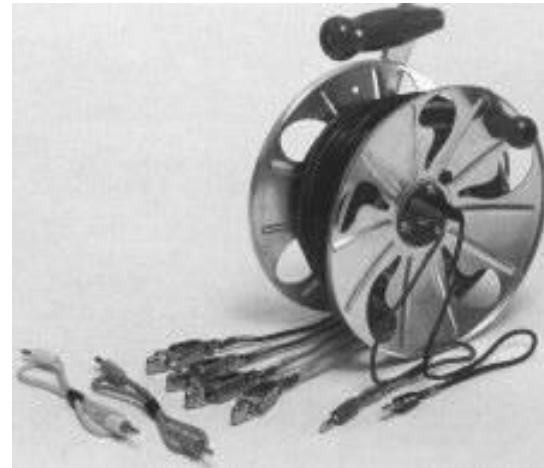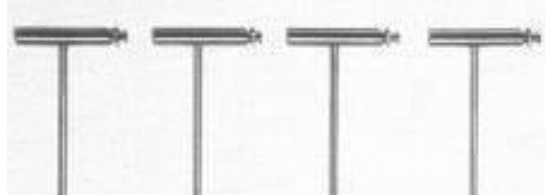

Soil Resistivity – Collins Rod



Resistivity - Soil Box



Conductivity

- **Opposite of resistivity**
- **Units - millimhos/cm or Siemens per meter (S/m)**
- **The term conductor is used to designate a member of an electrical circuit that easily carries an electrical current**



Conductance

- **Examples of conductors in corrosion control –**
 - **Wire or Cable**
 - **Pipes or other metallic structures**
- **Different metallic materials have different capabilities for carrying electric current. Related to the characteristic resistivity of the material discussed earlier**
- **Can water or soil be considered a conductor?**



Conductance



- Different materials have different conductivities, e.g.
 - Copper - 100%
 - Aluminum - 60
 - Magnesium - 36.8
 - Zinc - 27.6
 - Brass - 24.6
 - Steel - 9.6
 - Lead - 8.0



Conductance

- Although copper is the obviously the best conductor material, a steel pipe (even though a relatively poor conductor material) can be a very good practical conductor because, particularly in larger sizes, the amount of steel in the pipe is so much greater than the amount of copper in the usual copper wire or cable

Copper wire

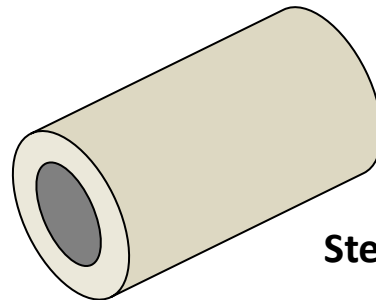
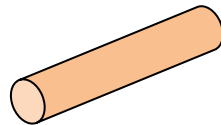


Steel pipe

Conductance

- **Example,**
 - Resistance of 1000 feet of 4/0 American Wire Gage (AWG) copper cable (approx 0.54 inch dia.) about 0.051 ohms
 - Resistance of 1000 feet of 12-inch steel pipe (0.375-inch wall thickness) about 0.0058 ohms i.e., approx one-tenth of the heavy copper cable

Copper cable

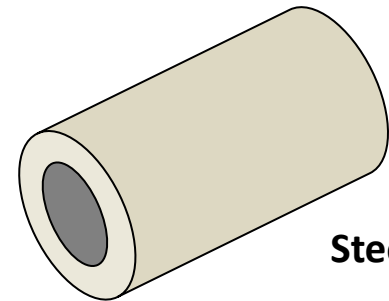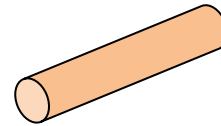

Steel pipe

Polarity

- The term polarity is important in determining the direction of conventional current flow in practical usage
- The direction of conventional current flow is “+” positive to “-” negative
- *In chapter 2*, flow of electrons is shown from minus (-) to plus (+) which is opposite to conventional current flow direction



Insulator

- Insulator or insulating material has very high resistance to the flow of electrical current and is used to confine or control the flow of current in electrical circuits

Examples:

- Wire or cable jackets of rubber
- Neoprene
- Plastics
- Fiberglass
- Coatings




Ohm's Law

- **Workers in the field of underground corrosion control must have thorough understanding of Ohm's Law as it applies to DC circuits**
- **Ohm's Law states that one volt will cause one ampere of current flow through a circuit whose resistance is one ohm**




Ohm's Law

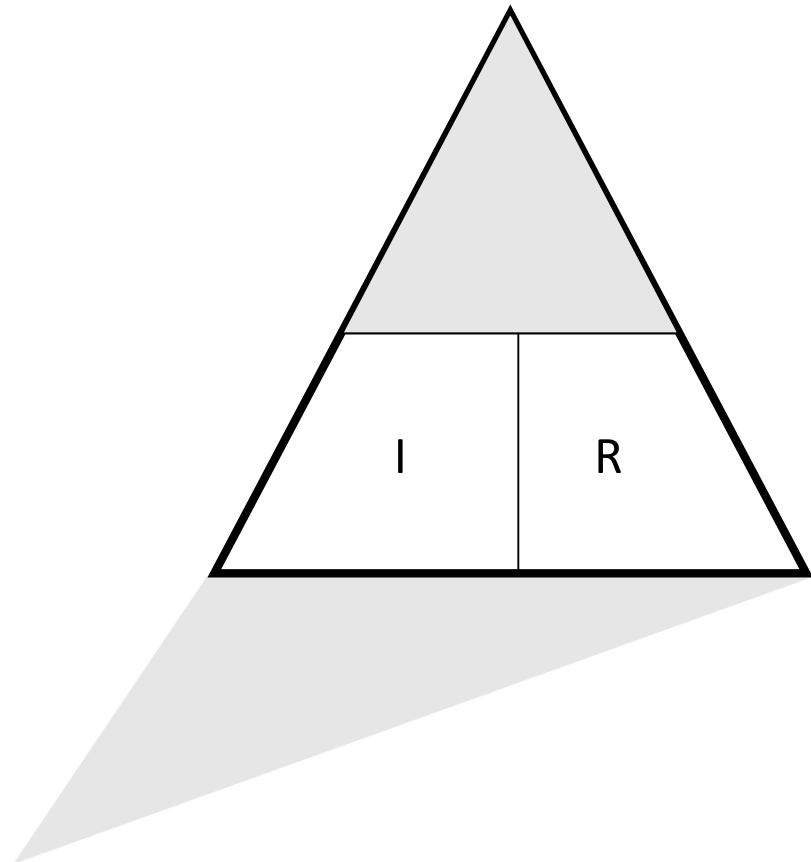- $E = I \times R$
- $I = E / R$
- $R = E / I$
 - E = Voltage
 - I = Current
 - R = Resistance
- **Power (Watts)**
- $P = E \times I$
- $P = I^2 \times R$
 - P = Power in watts
 - R = Resistance in ohms
 - E = Voltage in volts
 - I = Current in amperes




Ohm's Law

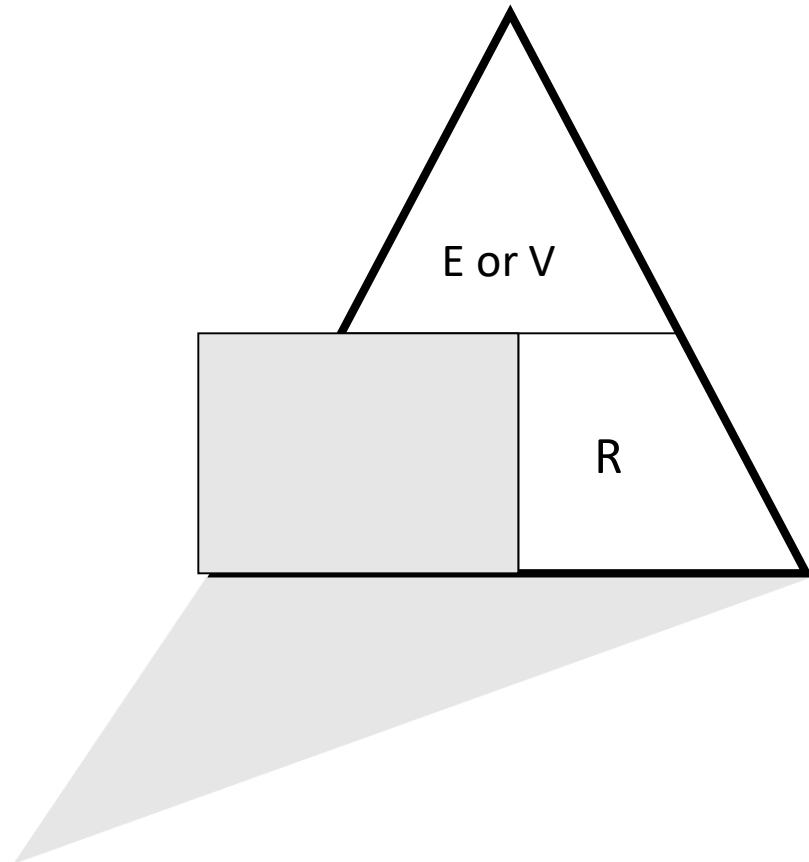- $E = I \times R$
- $I = E / R$
- $R = E / I$
 - E = Voltage
 - I = Current
 - R = Resistance
- Power (Watts)
- $P = E \times I$
- $P = I^2 \times R$
 - P = Power in watts
 - R = Resistance in ohms
 - E = Voltage in volts
 - I = Current in amperes




Ohm's Law

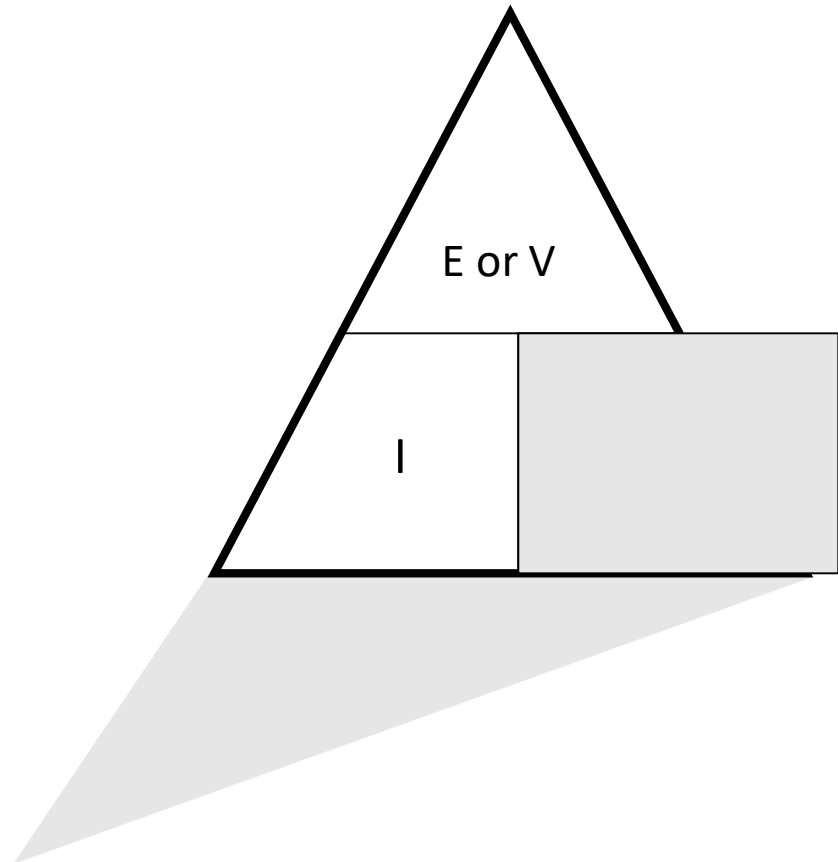- $E = I \times R$
- $I = E / R$
- $R = E / I$
 - E = Voltage
 - I = Current
 - R = Resistance
- Power (Watts)
- $P = E \times I$
- $P = I^2 \times R$
 - P = Power in watts
 - R = Resistance in ohms
 - E = Voltage in volts
 - I = Current in amperes




Ohm's Law

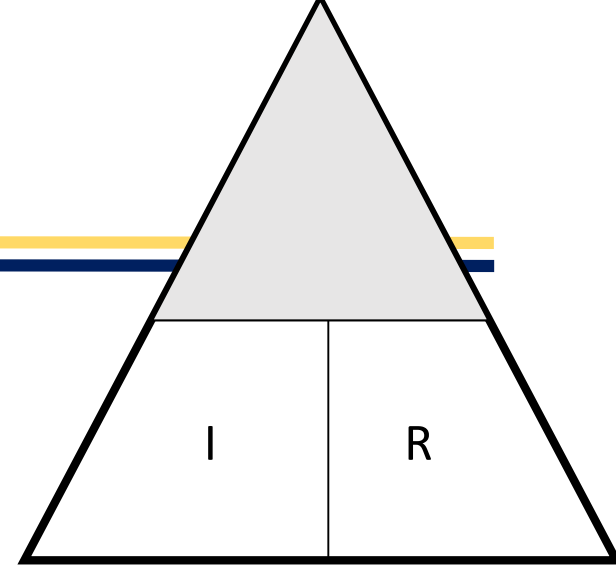- Assume,
 - Current, I , flowing through a circuit is 3.6 A
 - Circuit Resistance, R , is 1.7 Ω
 - What is the voltage = ?
 - $E = I \times R$
 -
 - Volts = 3.6 A x 1.7 Ω = 6.12 V
 - If any two components are known, the other can be calculated




Ohm's Law

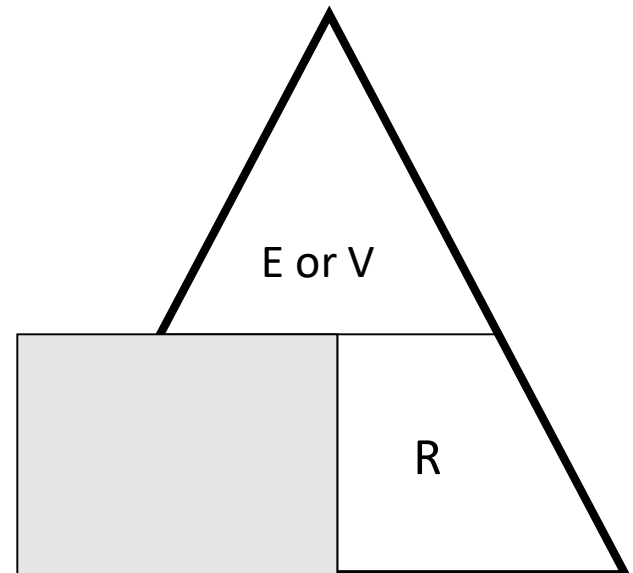- If $E = 12 \text{ V}$ and $R = 3.5 \text{ } \Omega$
- What is the current, I ?
- $I = \frac{E}{R} = \frac{12 \text{ V}}{3.5 \text{ A}}$
- Current, $I = 3.43 \text{ A}$



Ohm's Law

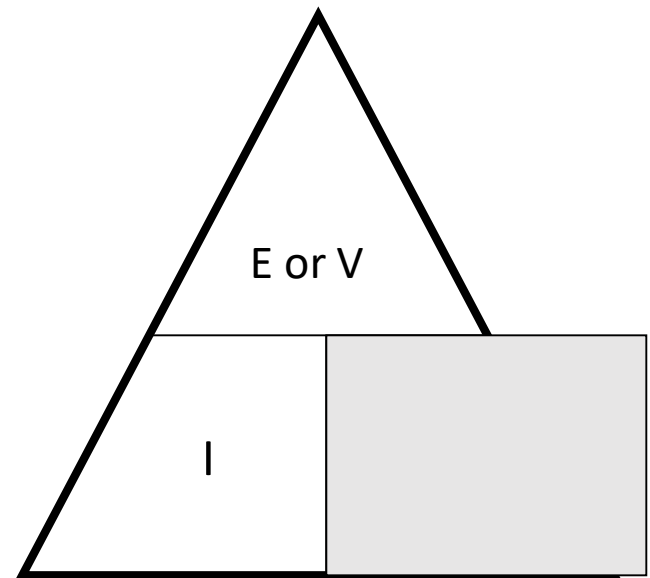- If $E = 6.0 \text{ V}$, $I = 1.5 \text{ A}$,
- What is the Resistance, R ?
- $R = \frac{E}{I} = \frac{6.0 \text{ V}}{1.5}$
- Resistance, $R = 4 \text{ } \Omega$



Ohm's Law - Caution

- Values entered in the formula must be in appropriate units
- For example,
 - Voltage circuit is 2.0 V and the current measured in the circuit is 1.0 mA
 - Do not mix up units
 - Resistance = $\frac{2.0 \text{ V}}{1.0 \text{ mA}} = 2 \Omega$ is **WRONG !**



Ohm's Law

- Either convert 1.0 mA to A

i.e., $\frac{1.0 \text{ mA}}{1000 \text{ mA}} = 0.001 \text{ A}$

- The correct calculation would then be,

- Resistance = $\frac{2 \text{ V}}{0.001 \text{ A}} = 2000 \Omega$

- Alternatively, convert V to mV


- Then, Resistance = $\frac{2000 \text{ mV}}{1.0 \text{ mA}} = 2000 \Omega$



Basic Electrical Circuit

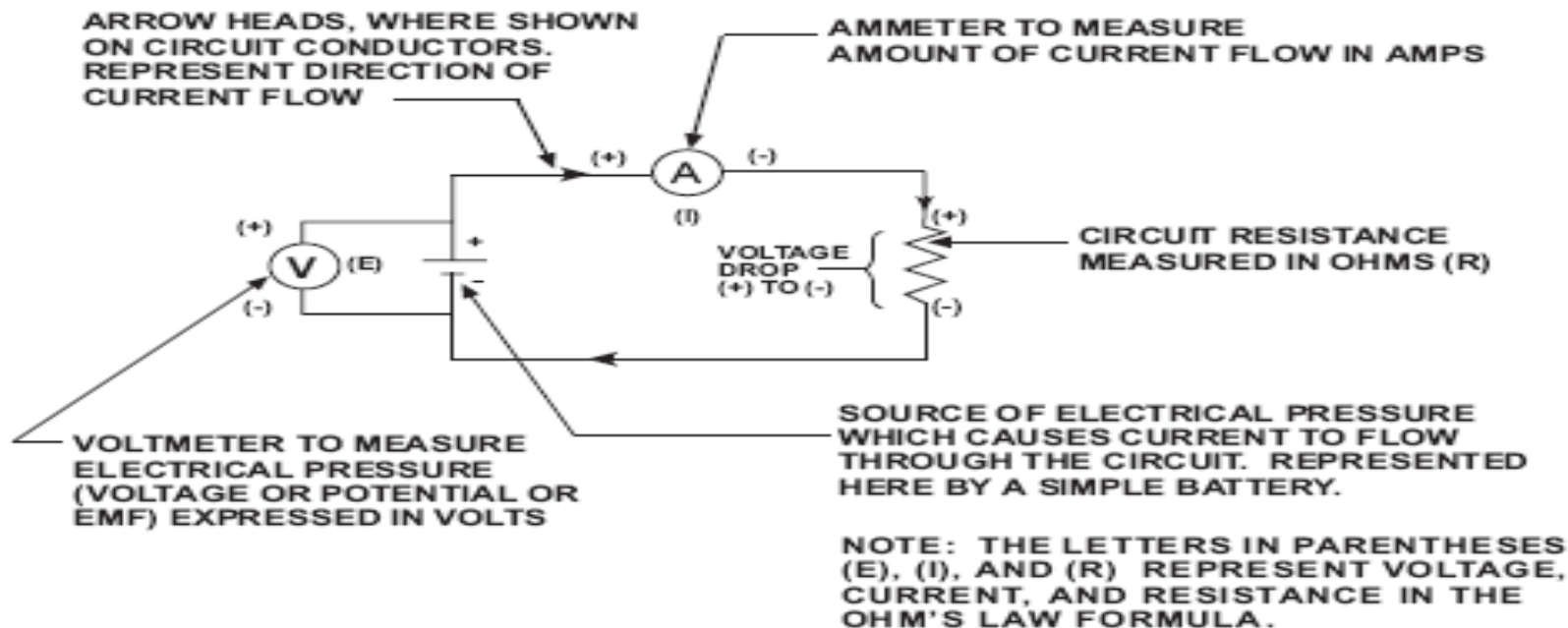- Figure 1-3 shows a simple circuit with a single resistor
- Assume that a DC power source providing current to a cathodic protection system for corrosion has instruments which indicate the following:
 - Supply voltage (E) is 20 V
 - Current flow (I) is 5 A
 - Circuit resistance (R) can be calculated using Ohm's law, $R = E/I$
 - Circuit Resistance = $20V/5A = 4 \text{ Ohms}$





**THE BASIC ELECTRICAL CIRCUIT
FIGURE 1-3**


Basic Electrical Circuit


- 20 V DC power source is connected across a known resistance of 4 Ω
- What is the current flow ?
- Can be calculated by using $I = E/R$
- Current Flow (I) = 20 V / 4 Ω = 5 A



The Series Electrical Circuit

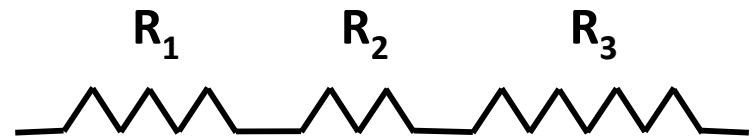- Figure 1-4 represents an electrical circuit where the total circuit resistance comprises 3 load resistances connected in series
- “Series” means that the load resistances are connected end-to-end and that the same amount of current passes through each of the resistances
- Total resistance is sum of all resistances in series
- $R_{\text{Total}} = R_1 + R_2 + R_3 + \dots$



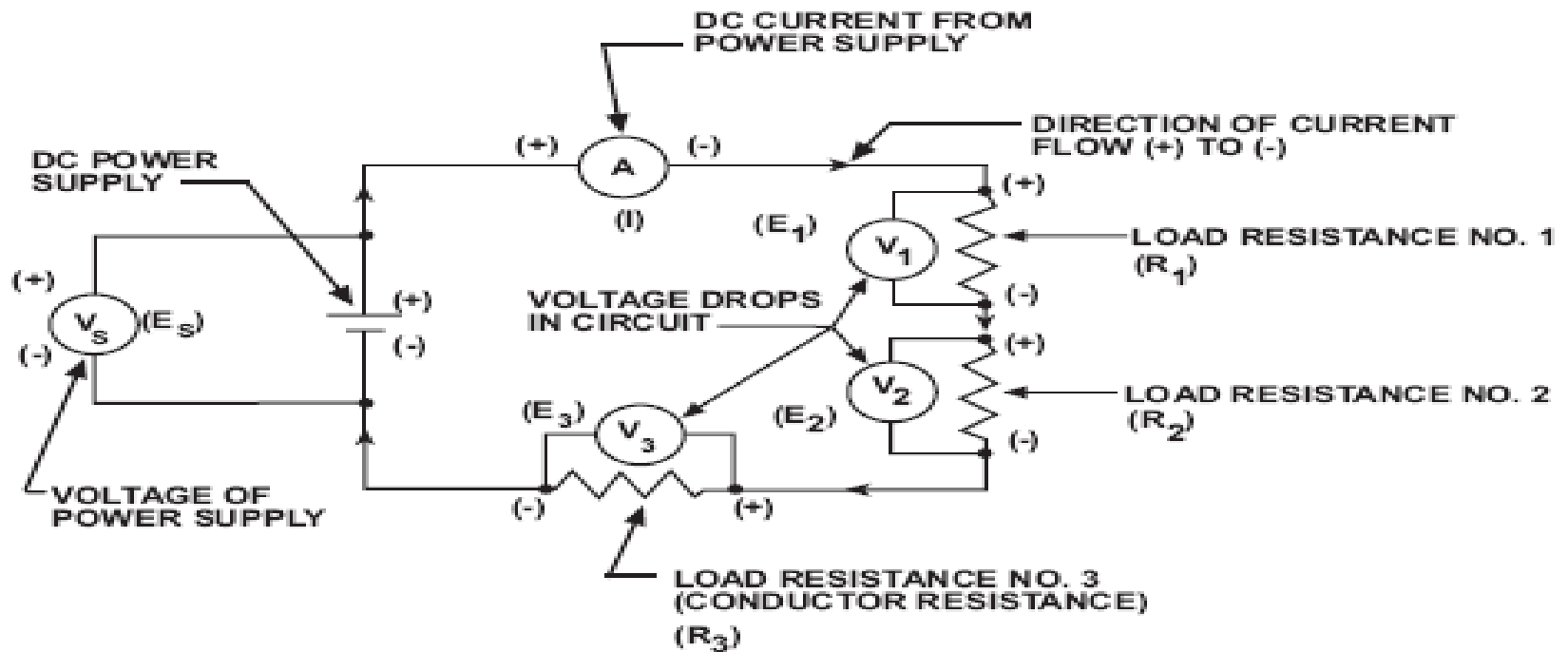

SERIES ELECTRICAL CIRCUIT

FIGURE 1-4

The Series Electrical Circuit

- Assume the following values for the circuit in figure 1-4
- Power supply voltage (E_s) = 10 V
- Circuit current flow (I) = 2.0 A
- Load resistance No. 1 (R_1) = 3.0 Ω
- Load resistance No. 2 (R_2) = 1.87 Ω
- Load resistance No. 3 (R_3) = 0.13 ohms
(20 ft of No. 8 wire)



Series Circuit

- Calculate the voltage drops across the three resistances
- Across R1: Voltage drop (V_1) = 2 A x 3.00 Ω = 6.0V
- Across R2: Voltage drop (V_2) = 2 A x 1.87 Ω = 3.74V
- Across R3: Voltage drop (V_3) = 2 A x 0.13 Ω = 0.26V

- Sum of these voltages is:
 $6.0 \text{ V} + 3.74 \text{ V} + 0.26 \text{ V} = 10 \text{ V}$
- Sum of the resistances is:
 $3.0 + 1.87 + 0.13 = 5 \text{ } \Omega$

- Check : $E = I \times R$



Series Electrical Circuit

- Assume the resistance values of R_1 , R_2 , and R_3 are unknown
- Power source voltage, $E_s = 10 \text{ V}$ and current, I , in the circuit is $= 2 \text{ A}$
- Determine the value of each resistor



Series Electrical Circuit

- **Measure the voltage drop across resistances R1 and R2 using a suitable DC voltmeter:**
 - **Measured voltage drop across resistance R1 = 6 V**
 - **Measured voltage drop across resistance R2 = 3.74 V**
 - **Calculated resistance R1 = 6 V / 2 A = 3 Ω**
 - **Calculated resistance R2 = 3.74 V / 2 A = 1.87 Ω**



Series Electrical Circuit

- Power source voltage (10V) and circuit current (2A) are known
- Using Ohm's law,
 - Total Circuit Resistance = $10 \text{ V} / 2 \text{ A} = 5 \Omega$
- Therefore, the value of resistance R3 is 5Ω minus the sum of R₁ and R₂
 - Resistance R3 = $5 - (3 + 1.87) = 0.13 \Omega$

Series Electrical Circuit

- Things to remember:
- Same amount of current flows from the power source through each resistance element in the circuit
- Sum of the voltage drops across the resistance elements in the circuit must equal the voltage of the power source
- Sum of resistance elements in the circuit must equal the total circuit resistance:


$$R_T = R_1 + R_2 + R_3 \dots\dots$$



Parallel Electrical Circuit

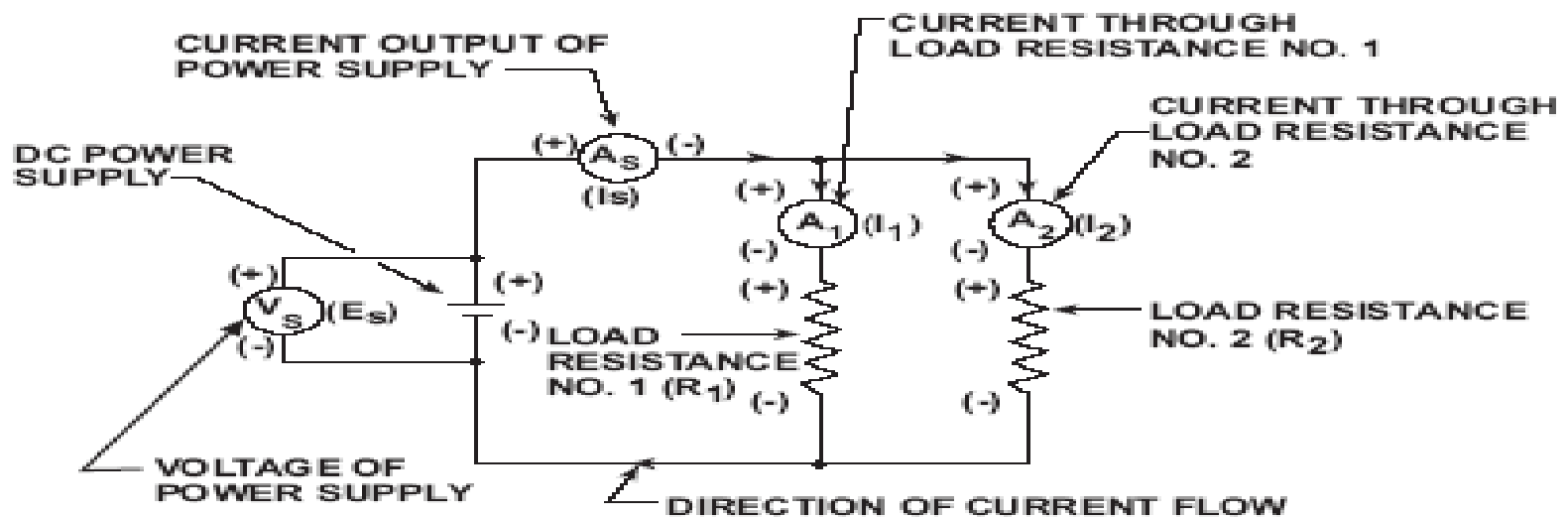- **Two or more load resistances are connected in parallel**
- **That is: + (current input) ends of all resistances are connected together instead of being connected end-to-end as is the case with a series circuit**
- **See Figure 1-5**





PARALLEL ELECTRICAL CIRCUIT
FIGURE 1-5

Parallel Electrical Circuit

- **Power source voltage is impressed on each resistance element instead of being distributed like in a series circuit**
- **Current is divided among the resistance branches**



The Parallel Electrical Circuit

- Assume the following:
- Power supply voltage (E_s) = 20 volts
- Power supply current (I_s) = 16.67 amps
- Load Resistance R_1 = 3 ohms
- Load Resistance R_2 = 2 ohms



The Parallel Electrical Circuit

- First calculate the current flow (I_1 and I_2) through resistances R_1 and R_2
- Voltage drop across each branch equals the power supply voltage (ES) = 20 V
- Current flow through R_1
 - $I_1 = 20 \text{ V} / 3 \text{ } \Omega = \underline{6.67 \text{ A}}$
- Current flow through R_2
 - $I_2 = 20 \text{ V} / 2 \text{ } \Omega = \underline{10 \text{ A}}$
- The sum of these two should equal the power source output current of 16.67 amps



The Parallel Electrical Circuit

- Second, calculate the parallel resistance of R_1 and R_2
- Parallel Resistance Formula, $R_{\text{Total}} = \frac{R_1 \times R_2}{R_1 + R_2}$
- $R_{\text{Total}} = \frac{3 \Omega \times 2 \Omega}{3 \Omega + 2 \Omega} = \frac{6}{5} = \underline{1.2 \Omega}$



Parallel Electrical Circuit

- Note that the parallel resistance, R_{Total} , of any two resistors is always less than the resistance of the smaller one
- Perform check, $R_{\text{Total}} = E_s / I_s$
- $R_T = 20 \text{ V} / 16.67 \text{ A} = \underline{\underline{1.2 \Omega}}$



The Parallel Electrical Circuit

- Parallel circuit resistance with more than two branches, can be calculated as follows:

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

The Parallel Electrical Circuits


- Remember the following important points:
 - Full power supply voltage is impressed across each parallel branch
 - Sum of the currents through the individual parallel branches must equal the total current output of the power source
 - Parallel resistance of two or more branches will always be less than that of the smallest branch resistance



Combination Circuits

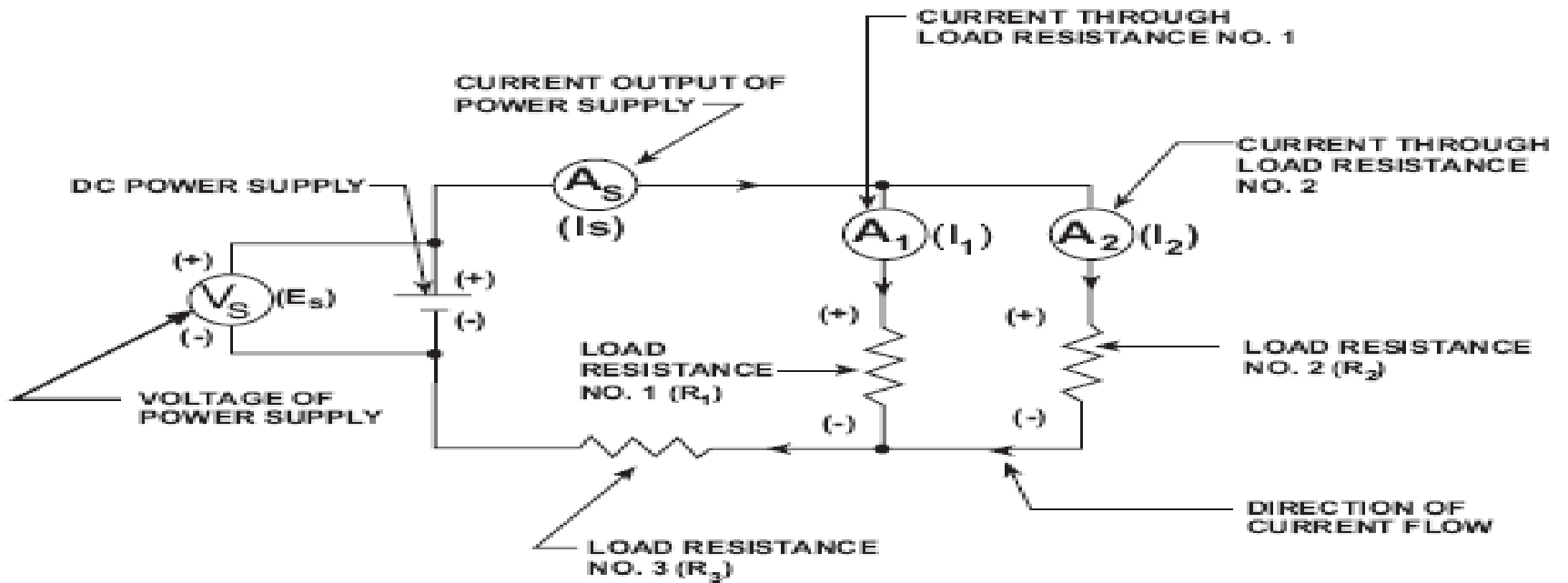- Circuits can be a combination of series elements and parallel elements
- See Figure 1-6





COMBINATION ELECTRICAL CIRCUIT

FIGURE 1-6

Combination Circuit

- The power supply output current divides between the two parallel branches R_1 and R_2 and then combines again after passing through these resistances
- The full power supply current then passes through the resistance element R_3
- Step 1: Calculate the effective resistance (R_p) of the parallel resistance elements, $1/R_p = 1/R_1 + 1/R_2$
- Step 2: Add that resistance to the series resistance elements to obtain total resistance, $R_{\text{Total}} = R_3 + R_p$



Combination Circuit

- Step 3: Calculate current flow, $I = V_S / R_{\text{Total}}$
This is the total current passing through R_1 and R_2 combined and also through R_3
- Step 4: Calculate voltage drop across R_3 , $V_3 = I \times R_3$
- Step 5: Calculate voltage drop across R_1 and R_2
It will be will be the same across each, $V_S - V_3$
- Step 6: Calculate current passing through R_1 and R_2 ,
 $I_1 = (V_S - V_3) / R_1$ and $I_2 = (V_S - V_3) / R_2$

Check: I must equal $I_1 + I_2$

